




# Basic Computer Architecture

## Chapter 8: Computer Arithmetic (Part I)
 
# Outline

- \* Addition
- \* Multiplication
- \* Division
- \* Floating Point Addition
- \* Floating Point Multiplication
- \* Floating Point Division



# Adding Two 1 bit Numbers

- \* Let us add two 1 bit numbers – **a** and **b**
  - \*  $0 + 0 = 00$
  - \*  $1 + 0 = 01$
  - \*  $0 + 1 = 01$
  - \*  $1 + 1 = 10$
- \* The **lsb** of the result is known, as the **sum**, and the **msb** is known as the **carry**

# Sum and Carry

$$\begin{array}{r} + \quad a \\ \quad b \\ \hline \end{array}$$

carry

sum

$a$	$b$	$s$	$c$
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1



Truth Table

$$s = a \oplus b = \bar{a}.b + a.\bar{b}$$

$$c = a.b$$
  
# Half Adder

- \* Adds two 1 bit numbers to produce a 2 bit result



# Full Adder



Add **three** 1 bit numbers to produce a 2 bit output

$$a + b + c_{in} = 2 * c_{out} + s$$

a	b	c <sub>in</sub>	s	c <sub>out</sub>
0	0	0	0	0
0	1	0	1	0
1	0	0	1	0
1	1	0	0	1
0	0	1	1	0
0	1	1	0	1
1	0	1	0	1
1	1	1	1	1

*S = 1 if  
Odd number of  
1s is present  
in the i/p*

  *c<sub>in</sub> = 1  
c<sub>out</sub> = 1*



$$s = \bar{a} b \bar{c}_{in} + a \bar{b} \bar{c}_{in} + \bar{a} \bar{b} c_{in} + a b c_{in}$$



S=1 if odd no of 1s in a, b, c<sub>in</sub>

# Equations for the Full Adder


$$\begin{aligned} s &= a \oplus b \oplus c_{in} \\ &= (a \cdot \bar{b} + \bar{a} \cdot b) \oplus c_{in} \\ &= (a \cdot \bar{b} + \bar{a} \cdot b) \cdot \overline{c_{in}} + \overline{a \cdot \bar{b} + \bar{a} \cdot b} \cdot c_{in} \\ &= a \cdot \bar{b} \cdot \overline{c_{in}} + \bar{a} \cdot b \cdot \overline{c_{in}} + \overline{(a \cdot \bar{b}) \cdot (\bar{a} \cdot b)} \cdot c_{in} \\ &= a \cdot \bar{b} \cdot \overline{c_{in}} + \bar{a} \cdot b \cdot \overline{c_{in}} + (\bar{a} + b) \cdot (a + \bar{b}) \cdot c_{in} \\ &= a \cdot \bar{b} \cdot \overline{c_{in}} + \bar{a} \cdot b \cdot \overline{c_{in}} + \bar{a} \cdot \bar{b} \cdot c_{in} + a \cdot b \cdot c_{in} \end{aligned}$$

$$c_{out} = \underbrace{a \cdot b} + \underbrace{a \cdot c_{in}} + \underbrace{b \cdot c_{in}}$$

# Circuit for the Full Adder

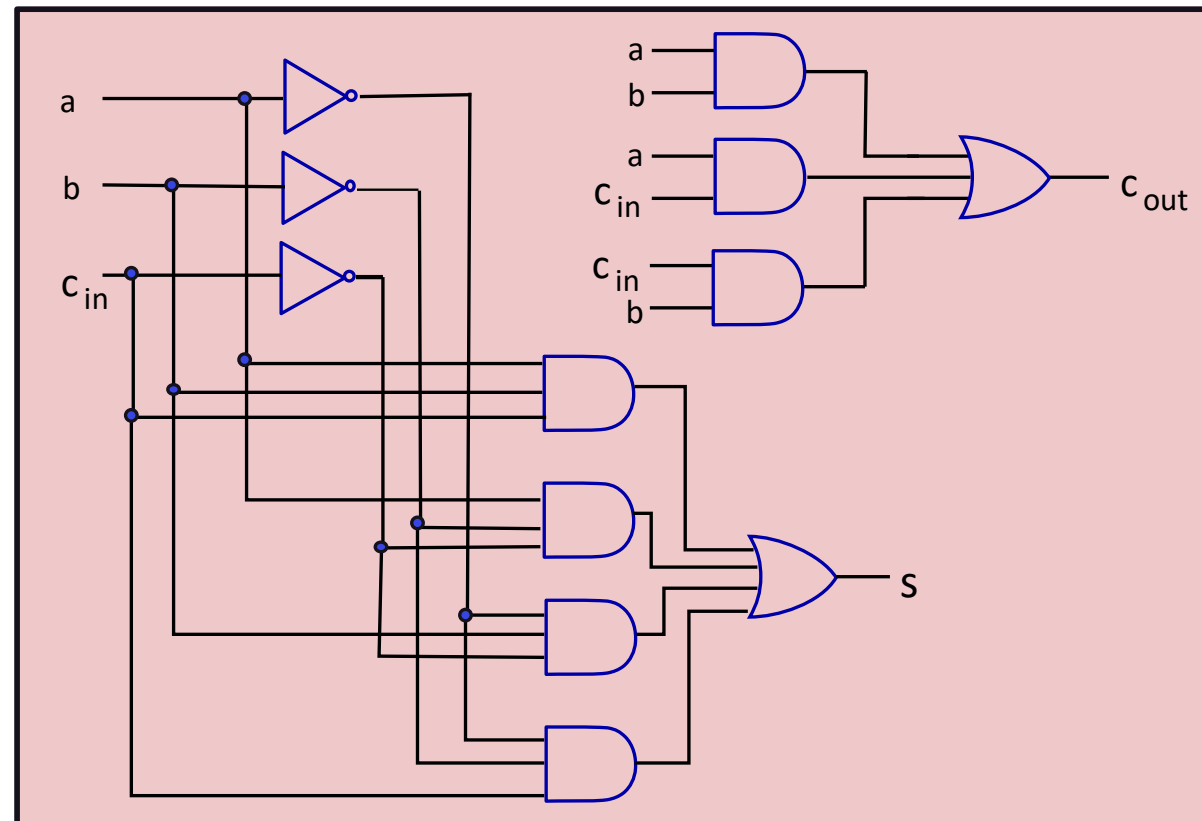 

# Addition of two $n$ bit numbers

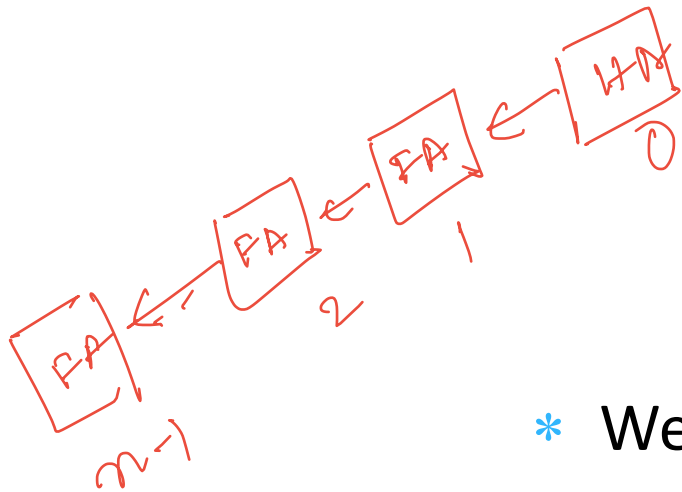

$$\begin{array}{r} \begin{array}{cccc} \boxed{1} & \boxed{1} & \boxed{1} & \boxed{1} \\ \downarrow & \downarrow & \downarrow & \downarrow \end{array} \\ + \begin{array}{r} 1011 \\ 0101 \\ \hline 10000 \end{array} \end{array}$$

The diagram shows the addition of two 4-bit numbers: 1011 and 0101. The result is 10000. Red circles highlight the carry bits: the four 1s in the top row, the 1s in the rightmost column of the second row, and the 1 in the leftmost column of the third row. Red arrows point from the carry bits in the second row to the carry-in of the next higher bit position in the third row.


- \* We start from the **lsb**
- \* Add the corresponding pair of bits and the **carry in**
- \* Produce a **sum bit** and a **carry out**

# Observations

- \* We keep adding pairs of bits, and proceed from the lsb to the msb
- \* If a carry is generated, we add it to the next pair of bits
- \* At the last step, if a carry is generated, then it becomes the msb of the result
- \* The carry effectively ripples through the bits
 
# Ripple Carry Adder

$t_w$   
 $t_f$   
 $(n-1)t_f + t_n$   
 $= O(n)$




c → carry



Full adder



Half adder

 

# Operation of the Ripple Carry Adder

- \* **Problem : Add A + B**
- \* Number the bits :  $A_1$  to  $A_n$  and  $B_1$  to  $B_n$ 
  - \* **lsb**  $\rightarrow A_1$  and  $B_1$
  - \* **msb**  $\rightarrow A_n$  and  $B_n$
- \* Use a **half adder** to add  $A_1$  and  $B_1$
- \* Send the carry(c) to a **full adder** that adds :  
 $A_2 + B_2 + c$
- \* Proceed in a similar manner **till the msb**

# How long does the Ripple Carry Adder take ?

- \* Time :
  - \* Time of half adder :  $t_h$
  - \* Time of full adder :  $t_f$
  - \* Total Time :  $t_h + (n-1)t_f$

# Asymptotic Time Complexity

- \* Most of the time, we are primarily interested in the **order of the function**
- \* For example : we are only interested in the  $n^2$  term in  $(2n^2 + 3n + 4)$
- \* We do not care about the **constants**, and terms with **smaller exponents**
  - \*  $3n$  and  $4$
- \* We can thus say that :
  - \*  $2n^2 + 3n + 4$  is order of  $(n^2)$

# The O notation

- \* Formally :
  - \* We say that:  $f(n) = O(g(n))$
  - \* if,  $|f(n)| \leq c|g(n)|$ , for all  $n > n_0$ . Here  $c$  is a positive constant.
- \* In simple terms:
  - \* Beyond a certain  $n$  ,  $g(n)$  is greater-than-equal to a certain constant times  $f(n)$ 
    - \* *For example, beyond 15,  $(n^2 + 10n + 16) \leq 2n^2$*


# Example of the big O Notation

$f(n) = 3n^2 + 2n + 3$ . Find its asymptotic time complexity.

**Answer:**

$$\begin{aligned} f(n) &= 3n^2 + 2n + 3 \\ &\leq 3n^2 + 2n^2 + 3n^2 \quad (n > 1) \\ &\leq 8(n^2) \end{aligned}$$

Hence,  $f(n) = O(n^2)$ .

 

$8n^2$  is a strict upper bound on  $f(n)$  as shown in the figure.

# Big O Notation - II



**Example:**

$f(n) = 0.00001n^{100} + 10000n^{99} + 234344$ . Find its asymptotic time complexity.

**Answer:**  $f(n) = O(n^{100})$

- \* We shall use the asymptotic time complexity metric (big O notation) to characterize the **time taken by different**


**adders**

  

# Ripple Carry Adders and Beyond

\* Time complexity of a ripple carry adder :

\*  $O(n)$

 

\*




Can we do better than  $O(n)$  ?

Step 2  
 $O(k)$



Step 2  
 $O\left(\frac{n}{k}\right)$

$O(k) + O\left(\frac{n}{k}\right)$

 
  
# Carry Select Adder $O(\sqrt{n})$ time

- \* Group bits into blocks of size (k)
- \* If we are adding two 32 bit numbers A and B, and  $k = 4$ , then the blocks are :



- \* Produce the result of each block with a **small ripple carry adder**

# Carry Select Adder - II

- \* In this case, the **carry propagates across blocks**
- \* Time complexity is  $O(n)$



Idea :

- \* Add the numbers in each block in parallel
- \* Stage I : For each **block**, produce **two results**
  - \* Assuming an **input carry of 0**
  - \* Assuming an **input carry of 1**

# Carry Select Adder – Stage II

- \* For each block we have two results available
- \* Result  $\rightarrow$  (k **sum** bits), and 1 **carry out** bit
- \* Stage II
  - \* Start at the **least significant block**
    - \* The input carry is 0
    - \* Choose the appropriate result from stage I
  - \* We now know the input carry for the second block
    - \* Choose the appropriate result
    - \* Result contains the input carry for the third block

# Carry Select Adder – Stage II

- \* Given the result of the second block
  - \* Compute the carry in for the third block
  - \* Choose the appropriate result
- \* Proceed till the last block
- \* At the last block (most significant positions)
  - \* Choose the correct result
  - \* The carry out value, is equal to the carry out of the entire computation.

# How much time did we take ?

- \* Our block size is  $k$ 
  - \* Stage I takes  $k$  units of time
- \* There are  $n/k$  blocks
  - \* Stage II takes  $(n/k)$  units of time

\* Total time :  $(k + n/k)$

$O(\sqrt{n})$

$$\frac{\partial (k + n/k)}{\partial k} = 0$$

$$\Rightarrow 1 - \frac{n}{k^2} = 0$$


$$\Rightarrow k = \sqrt{n}$$

# Time Complexity of the Carry Select Adder

- \*  $T = O(\sqrt{n} + \sqrt{n}) = O(\sqrt{n})$
- \* Thus, we have a  $\sqrt{n}$  time adder




Can we do better ?

 

*$O(\sqrt{2n}) + O(\sqrt{2n})$*
 
# Carry Lookahead Adder ( $O(\log n)$ )

- \* The main problem in addition is the **carry**
- \* If we have a mechanism to compute the **carry quickly**, we are done
- \* Let us thus focus on **computing the carry** without actually performing an addition



Generate Fun<sup>n</sup>

↓  
new carry  $g_i$

Propagate Fun<sup>n</sup>

↓  
carry to be propagated or not

$C_{in}$	0/1	0/1	0/1	0/1
$A_i$	0	1	0	1
$B_i$	0	0	1	1
$C_{out}$	0	0/1	0/1	1/1

$$g_i = \frac{A_i \cdot B_i}{1}$$


$$p_i = A_i \oplus B_i$$

$$C_{out}^i = g_i + p_i C_{in}^i$$
 
# Generate and Propagate Functions

A  
+B

- \* Let us consider two corresponding bits of A and B
  - \*  $A_i$  and  $B_i$
- \* **Generate function** : A new carry is **generated** ( $C_{out} = 1$ )



- \* **Propagate function** :  $C_{out} = C_{in}$
- \* **Generate and Propagate Functions are :**

$C_{in}$	-	0/1	0/1	0/1
$A_i$	0	0	1	1
$B_i$	0	1	0	1
$C_{out}$	0	0/1	0/1	1/1

$C_{out} = C_{in}$

$$g_i = A_i \cdot B_i$$

$$p_i = A_i \oplus B_i$$

XOR

$A_i$	$B_i$	$A_i \oplus B_i$
0	1	1
1	0	1

# Using the G and P Functions

- \* If we have the **generate** and **propagate** values for a bit pair, we can determine the **carry out**

$$C_{out} = g_i + p_i \cdot C_{in}$$

$$C_{out}^i = g_i$$

# Example

**Example:**

Let  $A_i = 0$ ,  $B_i = 1$ . Let the input carry be  $C_{in}$ . Compute  $g_i$ ,  $p_i$ , and  $C_{out}$ .

**Answer:**


$$g_i = A_i \cdot B_i = 0 \cdot 1 = 0$$

$$p_i = A_i \oplus B_i = 0 \oplus 1 = 1$$

$$C_{out} = g_i + p_i \cdot C_{in} = \underline{C_{in}}$$
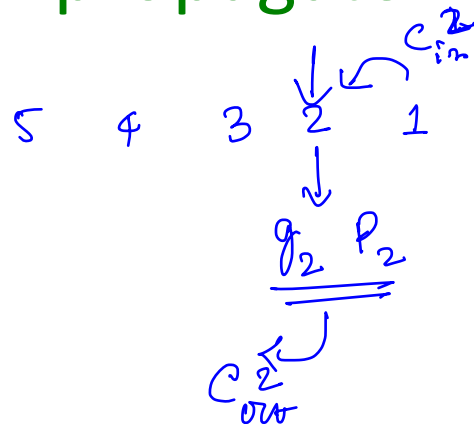
# G and P for Multi-bit Systems

- \*  $C_{\text{out}}^i \rightarrow$  **output carry** for  $i^{\text{th}}$  bit pair
- \*  $C_{\text{in}}^i \rightarrow$  **input carry** for  $i^{\text{th}}$  bit pair
- \*  $g_i \rightarrow$  **generate** value for  $i^{\text{th}}$  bit pair
- \*  $p_i \rightarrow$  **propagate** value for  $i^{\text{th}}$  bit pair




# G and P for Multibit Systems - II

$$C_{out}^1 = g_1 + p_1 \cdot C_{in}^1$$

$$\begin{aligned} C_{out}^2 &= g_2 + p_2 \cdot C_{out}^1 \\ &= g_2 + p_2 \cdot (g_1 + p_1 \cdot C_{in}^1) \\ &= (g_2 + p_2 \cdot g_1) + p_2 \cdot p_1 \cdot C_{in}^1 \end{aligned}$$
 
$$\begin{aligned} C_{out}^3 &= g_3 + p_3 \cdot C_{out}^2 \\ &= g_3 + p_3 \cdot ((g_2 + p_2 \cdot g_1) + p_2 \cdot p_1 \cdot C_{in}^1) \\ &= (g_3 + p_3 \cdot g_2 + p_3 \cdot p_2 \cdot g_1) + p_3 \cdot p_2 \cdot p_1 \cdot C_{in}^1 \end{aligned}$$



# G and P for multibit Systems - III

$$\begin{aligned} C_{out}^4 &= g_4 + p_4 \cdot C_{out}^3 \\ &= g_4 + p_4 \cdot (g_3 + p_3 \cdot g_2 + p_3 \cdot p_2 \cdot g_1) + p_3 \cdot p_2 \cdot p_1 \cdot C_{in}^1 \\ &= \underbrace{(g_4 + p_4 \cdot g_3 + p_4 \cdot p_3 \cdot g_2 + p_4 \cdot p_3 \cdot p_2 \cdot g_1)} + \underbrace{p_4 \cdot p_3 \cdot p_2 \cdot p_1 \cdot C_{in}^1} \end{aligned}$$

# Patterns

1 bit	$C_{out}^1 = \underbrace{g_1}_{G_1} + \underbrace{p_1}_{P_1} \cdot C_{in}^1$
2 bit	$C_{out}^2 = \underbrace{g_2 + p_2 \cdot g_1}_{G_2} + \underbrace{p_2 \cdot p_1}_{P_2} \cdot C_{in}^1$ ✓
3 bit	$C_{out}^3 = \underbrace{g_3 + p_3 \cdot g_2 + p_3 \cdot p_2 \cdot g_1}_{G_3} + \underbrace{p_3 \cdot p_2 \cdot p_1}_{P_3} \cdot C_{in}^1$
4 bit	$C_{out}^4 = \underbrace{g_4 + p_4 \cdot g_3 + p_4 \cdot p_3 \cdot g_2 + p_4 \cdot p_3 \cdot p_2 \cdot g_1}_{G_4} + \underbrace{p_4 \cdot p_3 \cdot p_2 \cdot p_1}_{P_4} \cdot C_{in}^1$
n bit	$C_{out}^n = G_n + P_n \cdot C_{in}^1$ ✓


↑

$$(g_n + p_n g_{n-1} + p_n p_{n-1} g_{n-2} + \dots)$$

$$P_n = p_n p_{n-1} p_{n-2} \dots p_1$$
 
# Computing G and P Quickly

- \* Let us **divide** a block of  $n$  bits into **two parts**




- \* Let the carry out and carry in be :  $C_{out}$  and  $C_{in}$

- \* We want to find the relationship between

- \*  $G_{1,n}, P_{1,n}$  and  $(G_{m+1,n}, G_{1,m}, P_{m+1,n}, P_{1,m})$
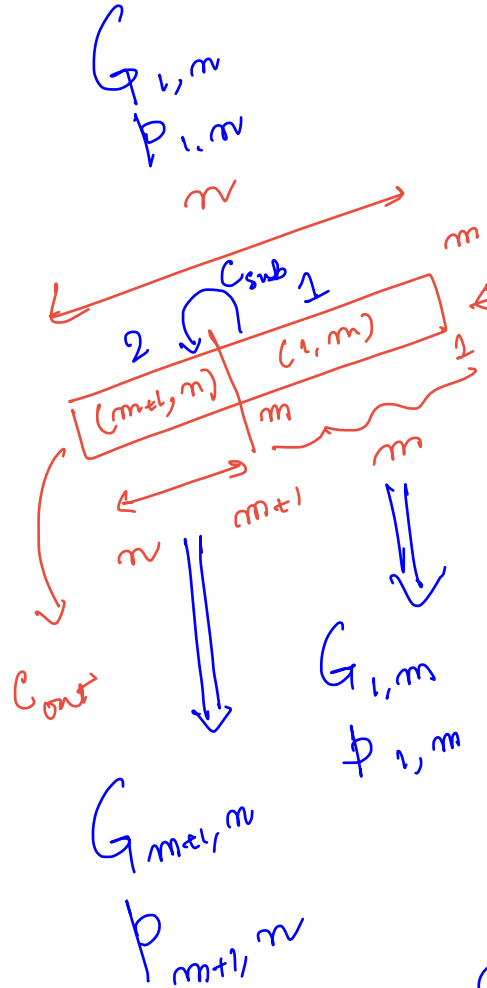
$$\begin{aligned}
 C_{out} &= G_{m+1,n} + P_{m+1,n} C_{sub} \\
 &= G_{m+1,n} + P_{m+1,n} (G_{1,m} + P_{1,m} C_{in}) \\
 &= G
 \end{aligned}$$



# Computing G and P Quickly - II

$$\begin{aligned}C_{out} &= G_{m+1,n} + P_{m+1,n} \cdot C_{sub} \\&= \underline{G_{m+1,n}} \\&+ P_{m+1,n} \cdot (G_{1,m} + P_{1,m} \cdot C_{in}) \\&= \underbrace{G_{m+1,n} + P_{m+1,n} \cdot G_{1,m}}_{G_{1,n}} + \underbrace{P_{m+1,n} \cdot P_{1,m}}_{P_{1,n}} \cdot C_{in}\end{aligned}$$

$$\underline{C_{out}} = \underline{G_{1,n}} + P_{1,n} \cdot C_{in} \quad \checkmark$$

$$\checkmark \quad \underline{G_{1,n}} = G_{m+1,n} + P_{m+1,n} \cdot G_{1,m} \quad \checkmark$$

$$\checkmark \quad P_{1,n} = P_{m+1,n} \cdot P_{1,m} \quad \checkmark$$

# Insight into Computing G and P quickly


## \* Insight :

- \* We can compute G and P for a large block
  - \* By first computing G and P for smaller sub-blocks
  - \* And, then **combining the solutions** to find the value of G and P for the larger block
- \* Fast algorithm to compute G and P
  - \* Use **divide-and-conquer**
  - \* Compute G and P functions in  $O(\log(n))$  time

# Carry Lookahead Adder – Stage I

- \* **Compute** G and P functions for all the blocks
- \* **Combine** the solutions to find G and P functions for sets of **2 blocks**
- \* **Combine** the solutions to find G and P functions for sets of **4 blocks**
- \* ....
- \* ....
- \* **Find the G and P functions for a block of size : 32 bits**

# Carry Lookahead Adder – Stage I

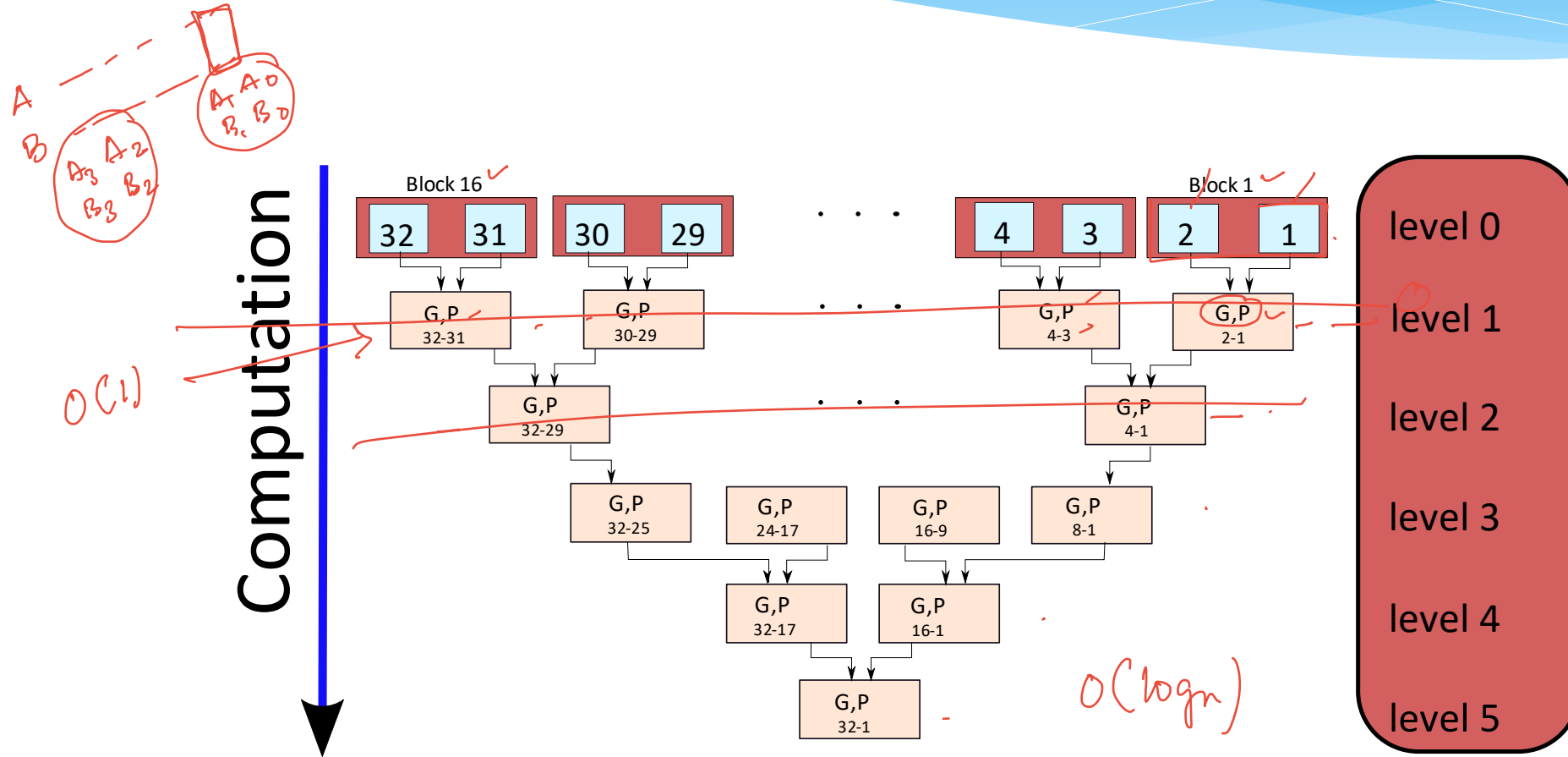


# CLA Adder – Stage I

- \* Compute G, P for **increasing sizes** of blocks in a **tree like fashion**
- \* **Time taken :**
  - \* Total :  $\log(n)$  levels
  - \* Time per level :  $O(1)$
  - \* Total Time :  $O(\log(n))$

# CLA Adder – Stage II

Block 1  
A<sub>1</sub> A<sub>0</sub>  
B<sub>1</sub> B<sub>0</sub>

Computation

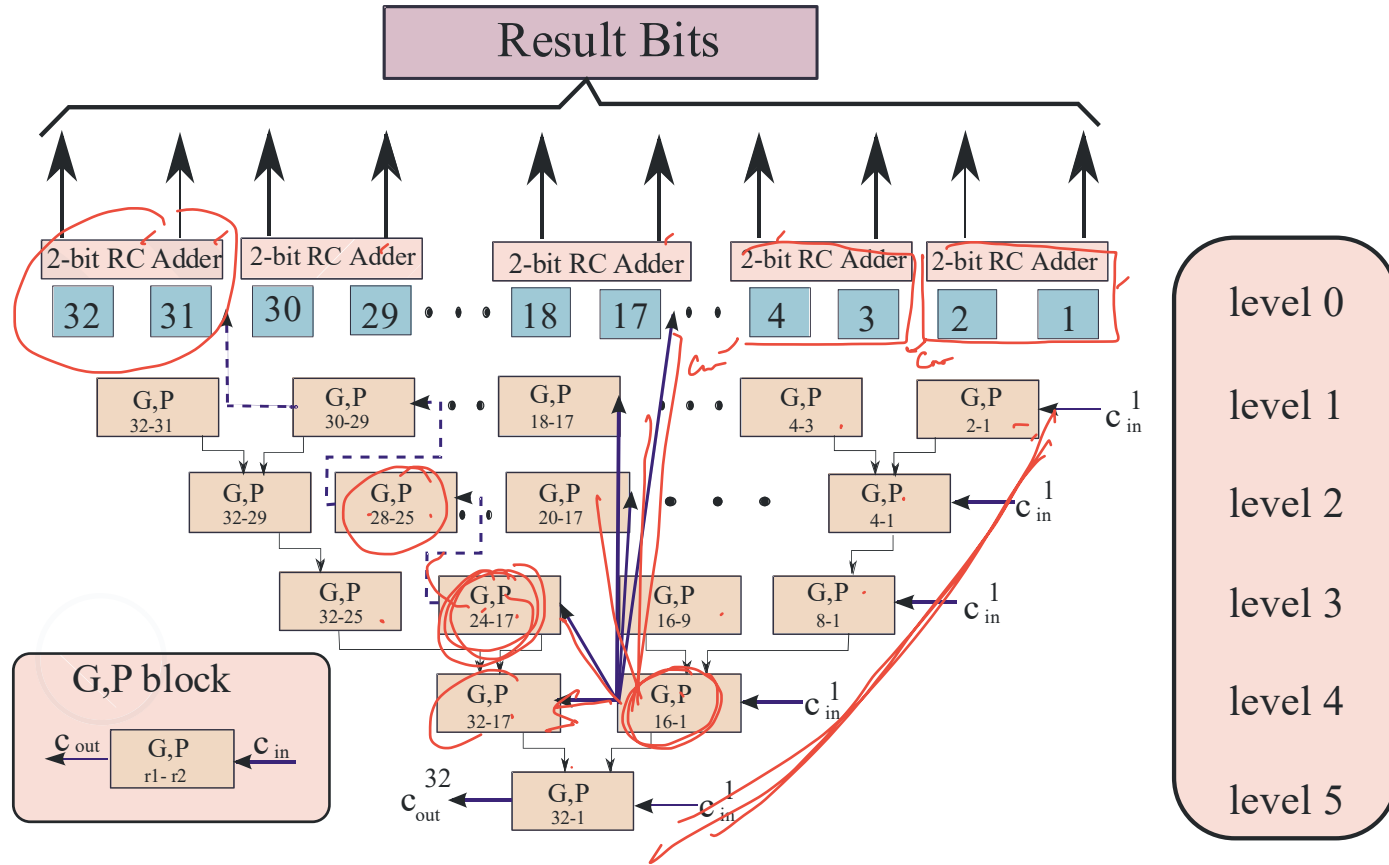

$(P_{21}, P_1)$   
24 17

$(P_{31}, P_{2+1})$   
28


# Connection of the G,P Blocks

- \* Each G,P block represents a range of bits  $(r_2, r_1)$  ( $r_2 > r_1$ )
  - \* The  $(r_2, r_1)$  G,P block is connected to all the blocks of the form  $(r_3, r_2+1)$
  - \* The carry out of one block is an input to all the blocks that it is connected with
- \* Each block is connected to another block at the same level, and to blocks at lower levels

# Operation of CLA – Stage II

- \* We start at the ~~leftmost~~ <sup>right</sup> blocks in each level
  - \* We feed an input carry value of  $C_{in}^1$
  - \* Each such block computes the output carry, and sends it to all the blocks that it is connected to
- \* Each connected block
  - \* Computes the output carry ✓
  - \* Sends it to all the blocks that it is connected to ✓
- \* The carry propagates to all the 2 bit RC adders

# CLA Adder – Stage II

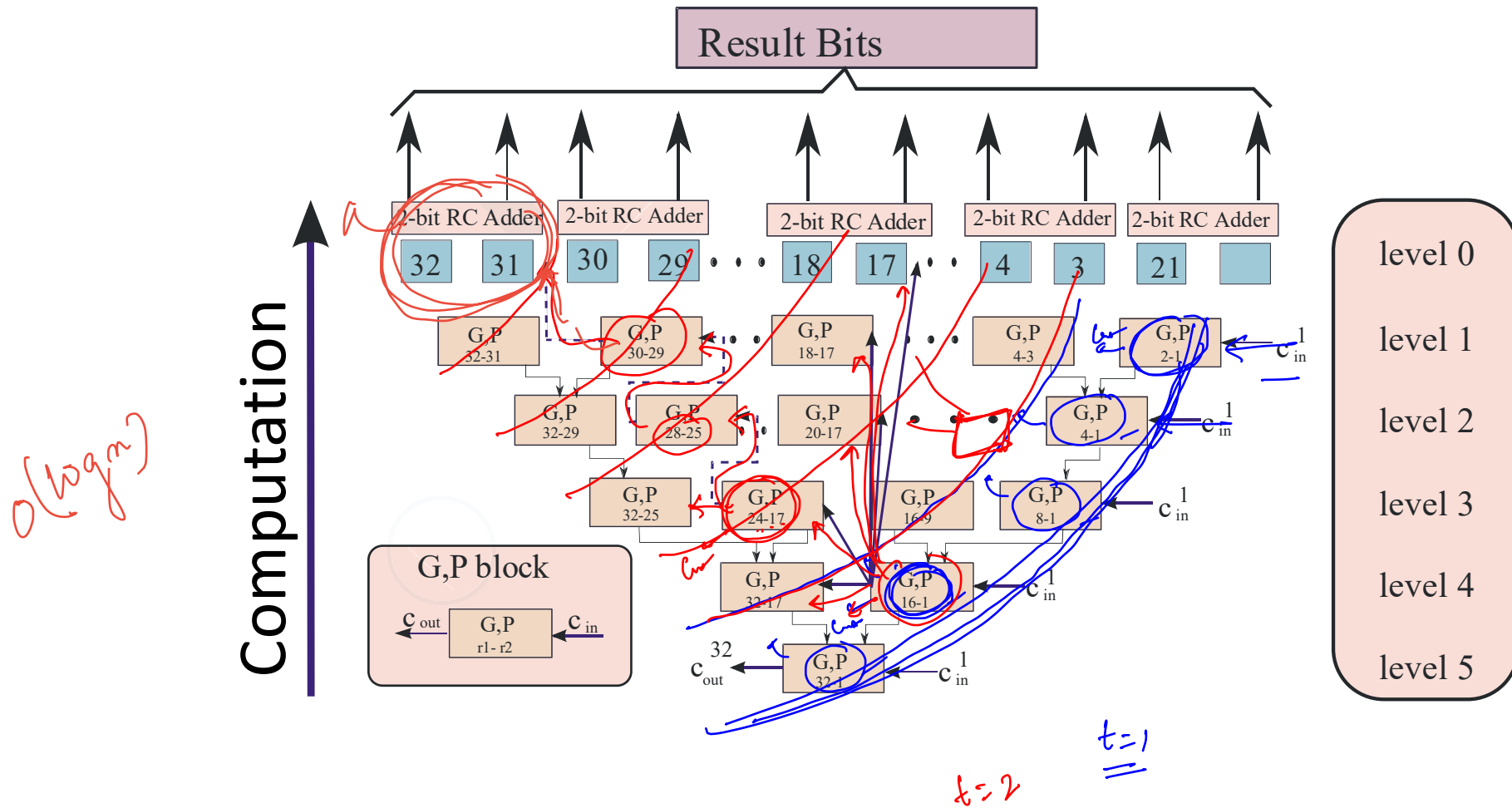

# Time Complexity

- \* In a similar manner, the **carry propagates** to all the RC adders at the zeroth level
- \* Each of them **compute the correct result**
- \* Time taken by Stage II :
  - \* Time taken for a carry to propagate from the (16,1) node to the RC adders
  - \*  $O(\log(n))$
- \* Total time :  $O(\log(n) + \log(n)) = O(\log(n))$



Time complexities of different adders:

- Ripple Carry Adder:  $O(n)$
- Carry Select Adder:  $O(\sqrt{n})$
- Carry Lookahead Adder:  $O(\log(n))$

# Outline

- \* Addition
- \* Multiplication
- \* Division
- \* Floating Point Addition
- \* Floating Point Multiplication
- \* Floating Point Division

